

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations



Tutorial of JWG-B2/B4/C1.17 on HVDC Transmission Systems –
Design and Economics
Converter Configurations – John Graham, ABB Brasil

john.graham@br.abb.com



Converter Configurations : Introduction

To start discussing **converter configurations** we need to consider:

- 1. Line configuration, bipolar or monopolar**
- 2. Transmitted power and voltage**
- 3. Location, especially regarding transportation**



While many configurations are possible, we discuss in detail only those applicable to overhead line transmission.

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




Variant	Tower Configuration	Remaining Transmission Capacity		Tower breakage	Relative cost %
		Ground return permitted			
		permitted	not permitted		
Single monopolar line		0	0	0	85
single bipolar line		50 (100)	0	0	100
double bipolar line		100	100	0	114
Two monopolar lines		50 (100)	0	50 (100)	126
two lines (bipolar or homopolar)		100	100	100	136

Cigré Technical Brochure 186 from WG 14.20 - 2001

STUDY COMMITTEE B2, JWG B2-17/B4/C1

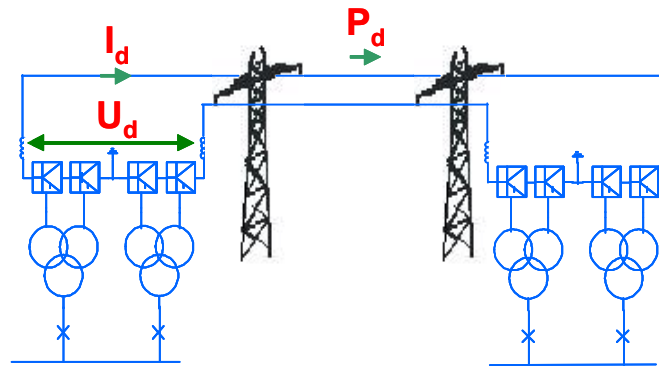
HVDC Transmission Configurations and Intermediate Stations




In all CSC cases, bi-polar operation only considered, except in emergency or maintenance.

STUDY COMMITTEE B2, JWG B2-17/B4/C1

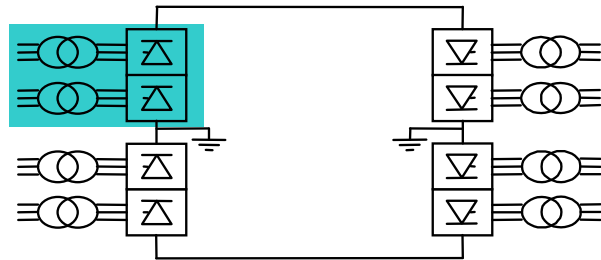
HVDC Transmission Configurations and Intermediate Stations



Bipole

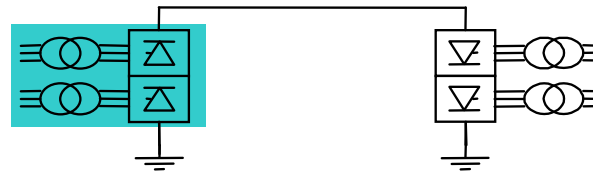


Monopole

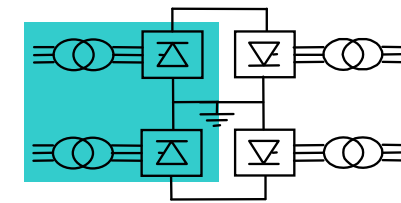


Back-to Back

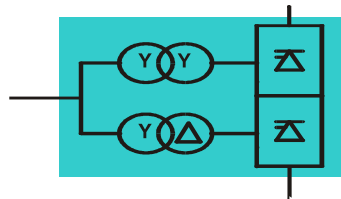
In all CSC cases, 12-pulse converters only considered



HVDC Classic

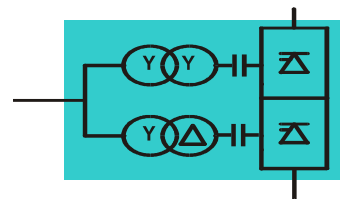


HVDC CCC

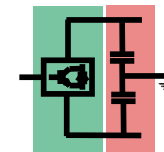

HVDC VSC

STUDY COMMITTEE B2, JWG B2-17/B4/C1

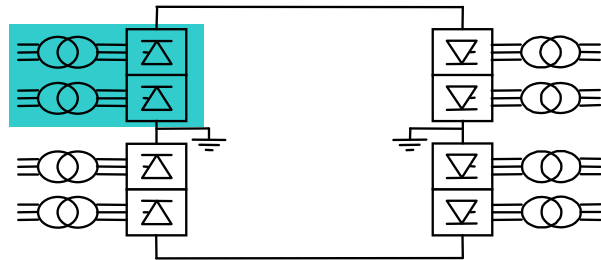
HVDC Transmission Configurations and Intermediate Stations



Bipole



Monopole

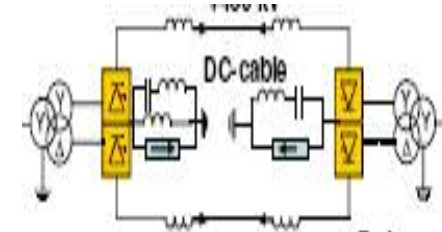

12-pulse centre-tap

In all CSC cases, bi-polar operation only considered, except in emergency or maintenance.

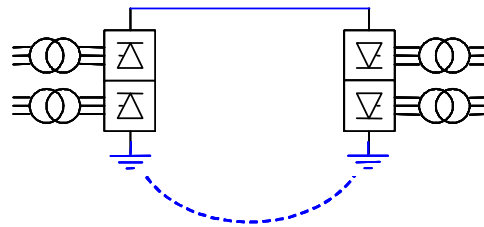


Figure 3.2.a Ground Return

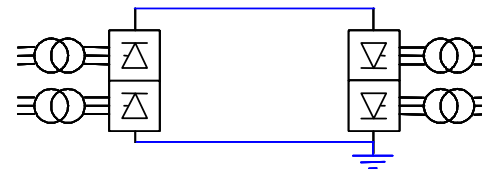


Figure 3.2.b Metallic Return




Basic types of Converters

- Naturally commutated converters (Thyristors)
(current source converters : CSCs)
 - Classic HVDC Transmission
Itaipu, Three Gorges, Baltic Cable, (many)
 - Capacitor Commutated Converters (CCC)
Garabi, Rapid City
- Voltage source converters (VSCs)
 - HVDC Light, HVDC Plus (IGBT)
Cross Sound, Murray Link, Troll A
 - VSC using GTO (statcom or industrial)

STUDY COMMITTEE B2, JWG B2-17/B4/C1

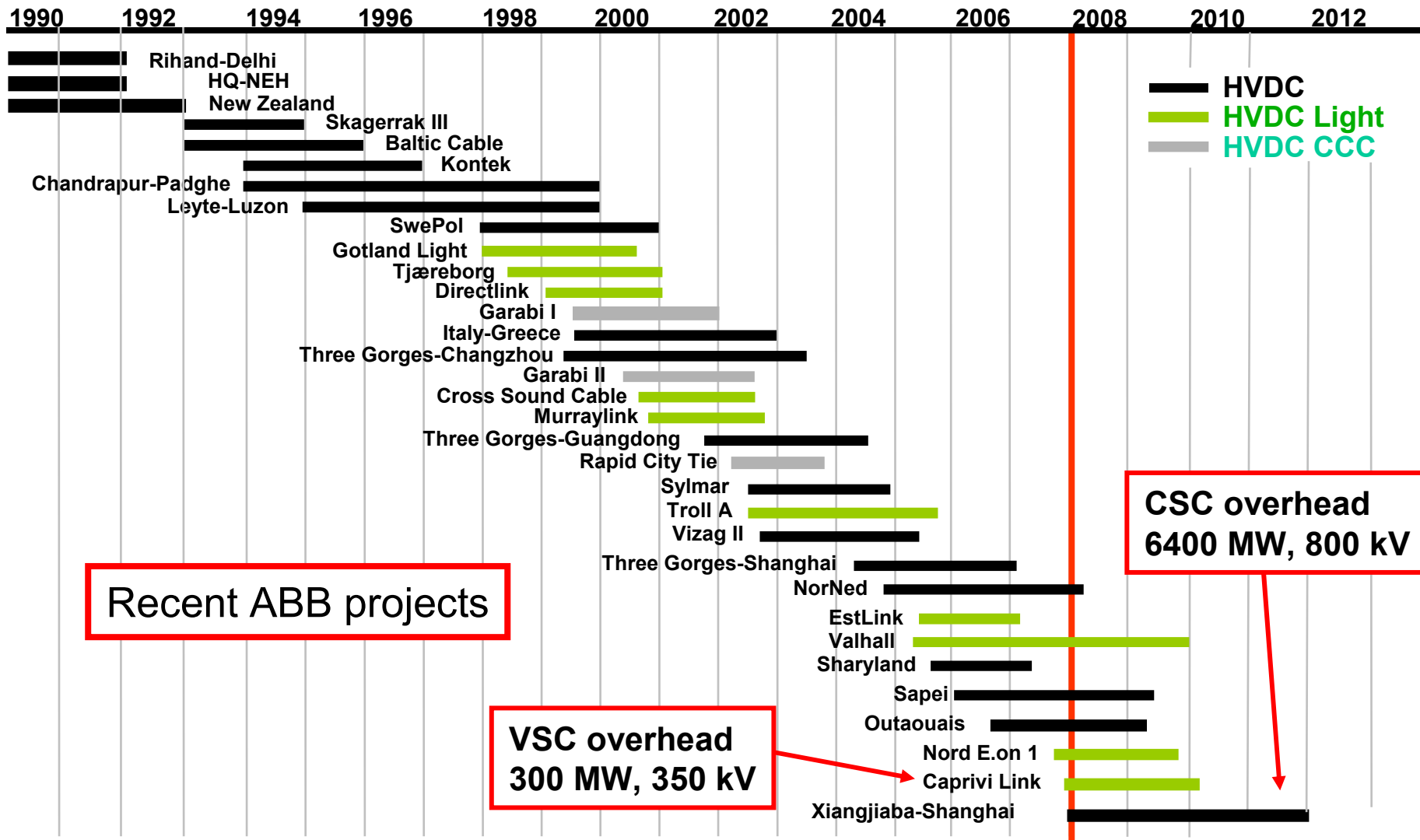HVDC Transmission Configurations and Intermediate Stations




Recent ABB projects

VSC overhead
300 MW, 350 kV

CSC overhead
6400 MW, 800 kV


STUDY COMMITTEE B2, JWG B2-17/B4/C1

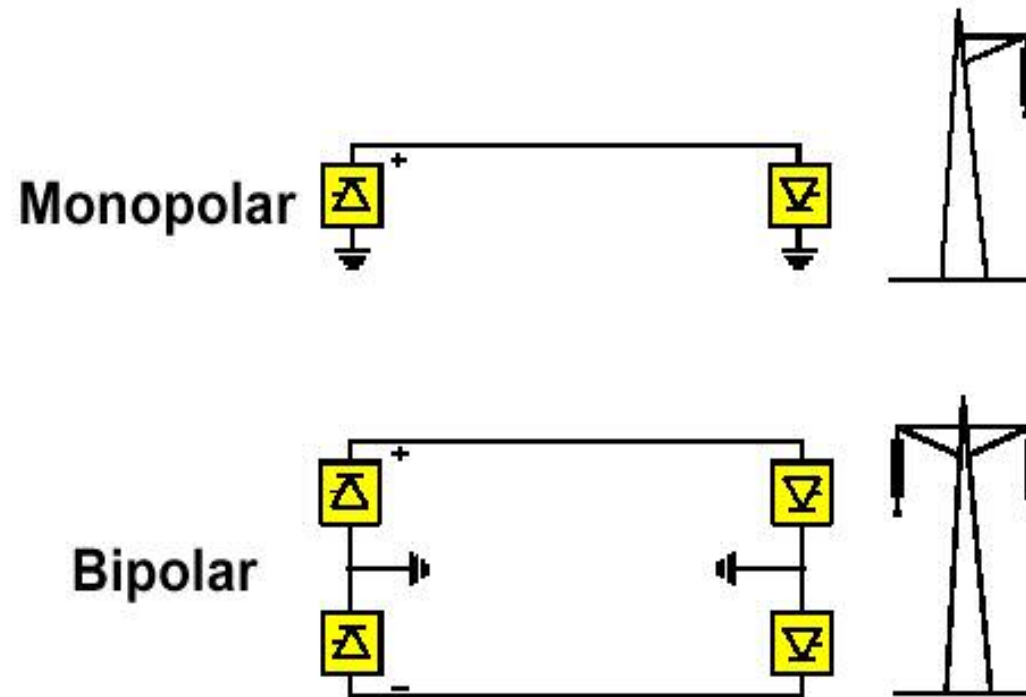HVDC Transmission Configurations and Intermediate Stations



STUDY COMMITTEE B2, JWG B2-17/B4/C1

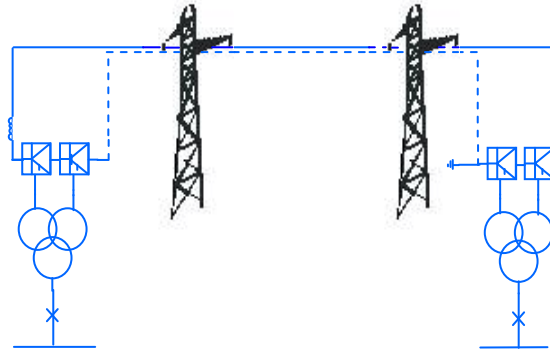
HVDC Transmission Configurations and Intermediate Stations



Investment Cost	+
Losses	-
Availability	-

STUDY COMMITTEE B2, JWG B2-17/B4/C1

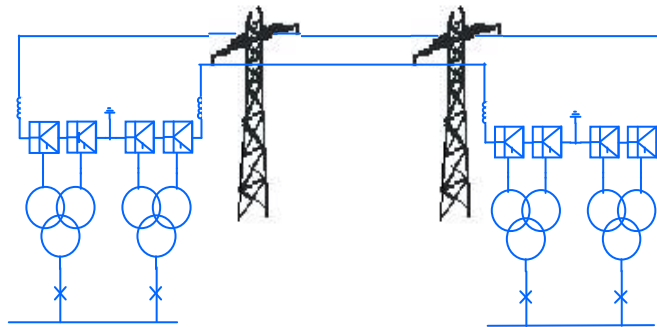HVDC Transmission Configurations and Intermediate Stations




Availability	+
Losses	+
Investment Cost	0

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




Phase 1

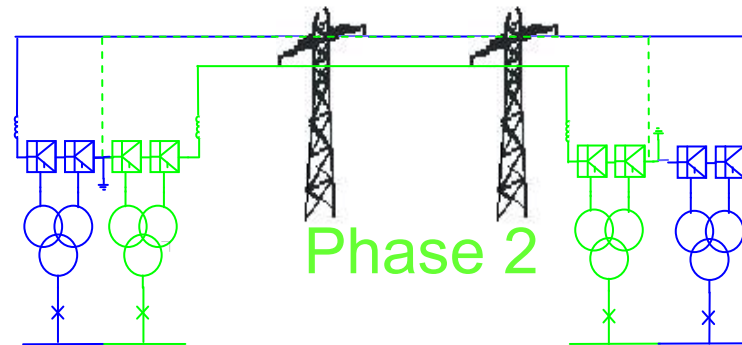

Investment Cost	+
Losses Phase 1	-
Availability Phase 1	-

STUDY COMMITTEE B2, JWG B2-17/B4/C1

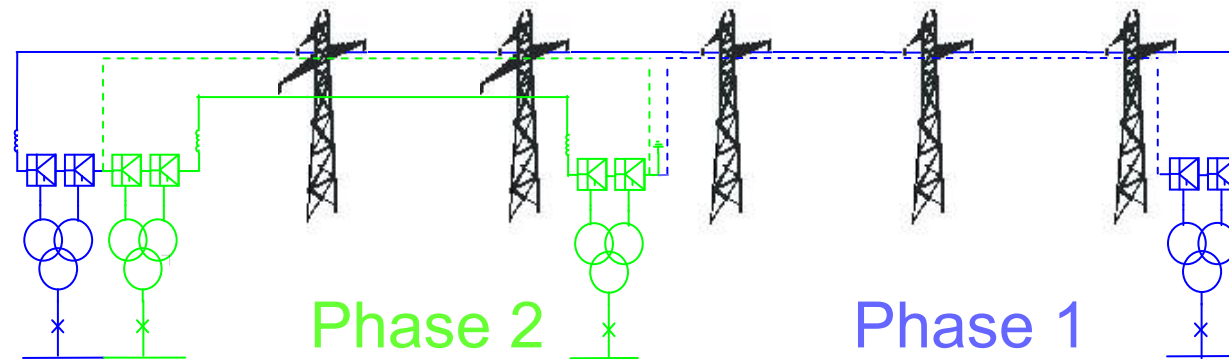
HVDC Transmission Configurations and Intermediate Stations



Investment Cost	+
Losses	-
Availability	-

STUDY COMMITTEE B2, JWG B2-17/B4/C1

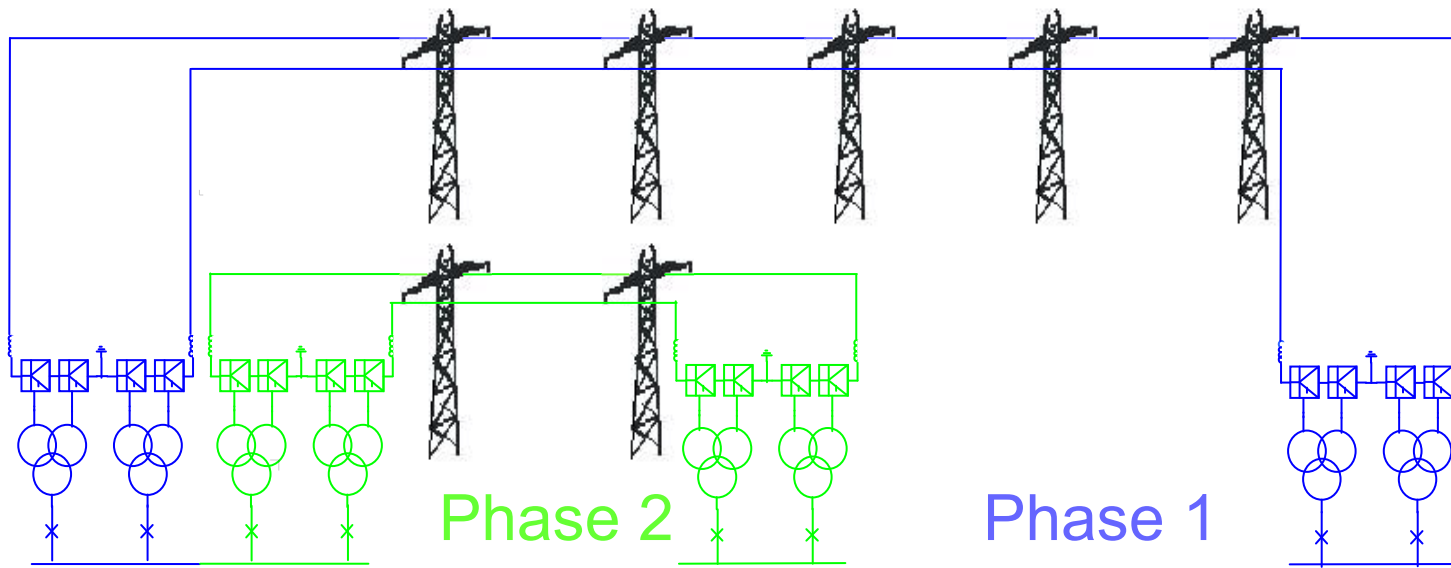
HVDC Transmission Configurations and Intermediate Stations



Investment Cost	-
Losses	+
Availability	+

STUDY COMMITTEE B2, JWG B2-17/B4/C1

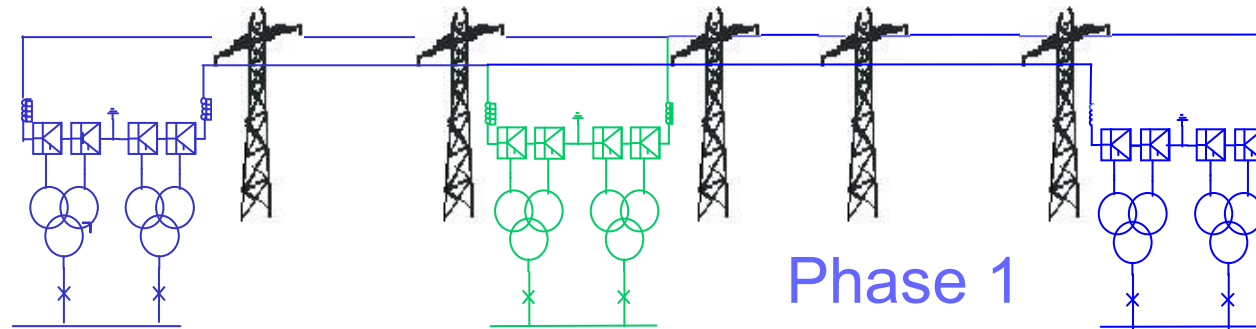HVDC Transmission Configurations and Intermediate Stations






Initial rating ?

Phase 2

Investment Cost: line/stations	+/o
Losses	+
Availability	o

STUDY COMMITTEE B2, JWG B2-17/B4/C1

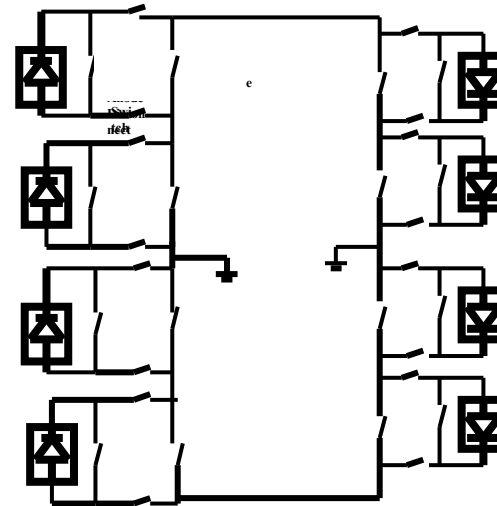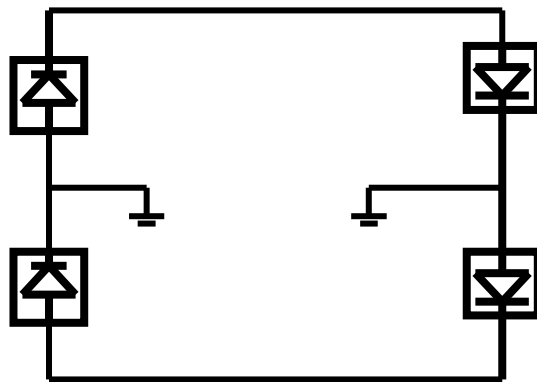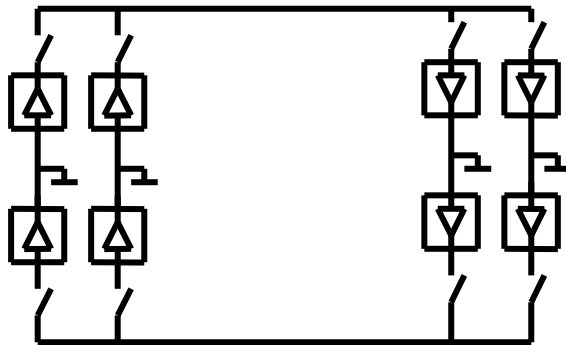
HVDC Transmission Configurations and Intermediate Stations



Configurations for maximum power
Transport restrictions on transformers
are normally limiting

STUDY COMMITTEE B2, JWG B2-17/B4/C1

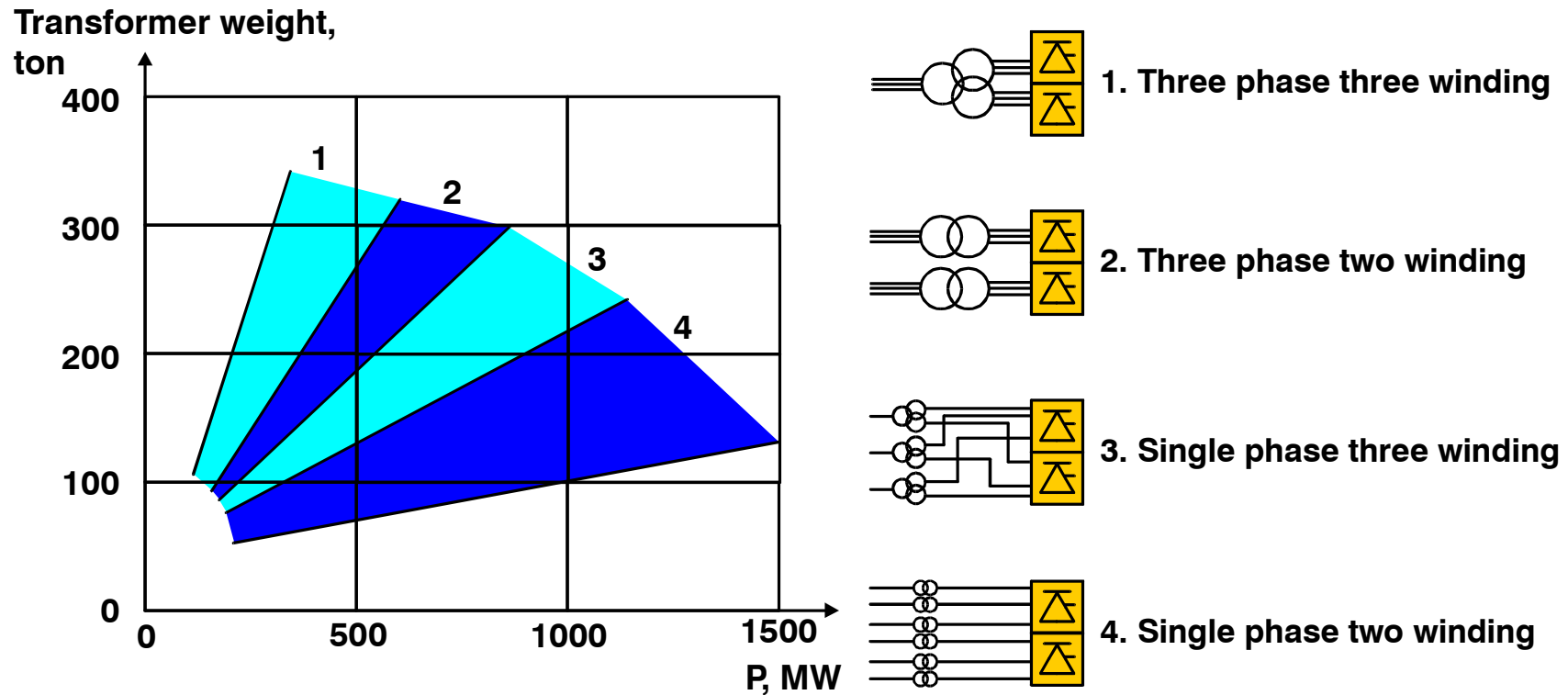
HVDC Transmission Configurations and Intermediate Stations



- The transformer topology is adopted to the requirements:
 - Size influences choice of topology (power and voltage increase size)
 - Spares strategy influences choice of topology

STUDY COMMITTEE B2, JWG B2-17/B4/C1

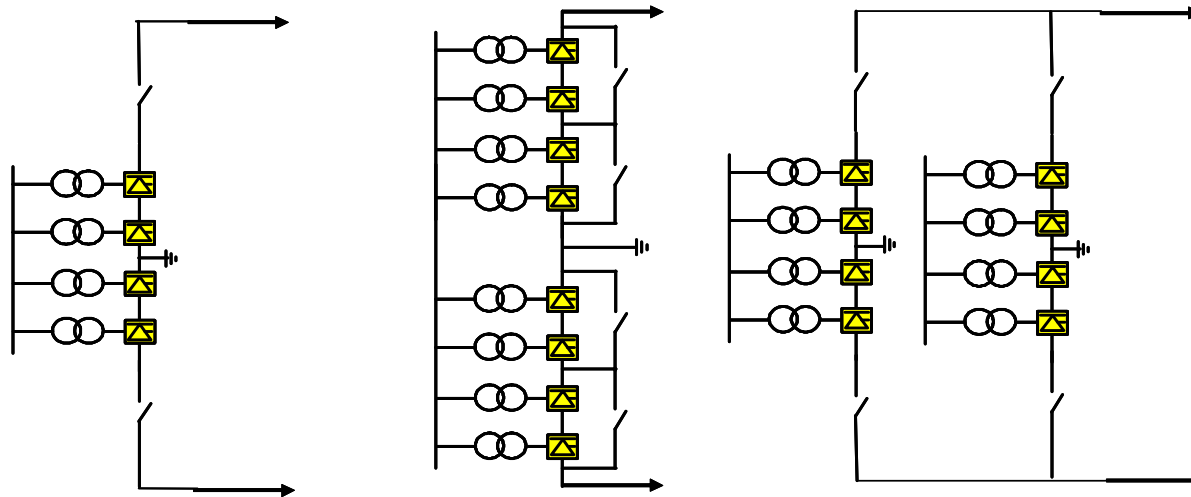HVDC Transmission Configurations and Intermediate Stations



One converter per pole, 3000 MW, Two converters, 6000 MW Two parallel, 6000 MW
Figure 3.3 Basic station configurations for 12-pulse converters


- The transformer topology is adopted to the requirements
- Valve current rating may determine parallel converters

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




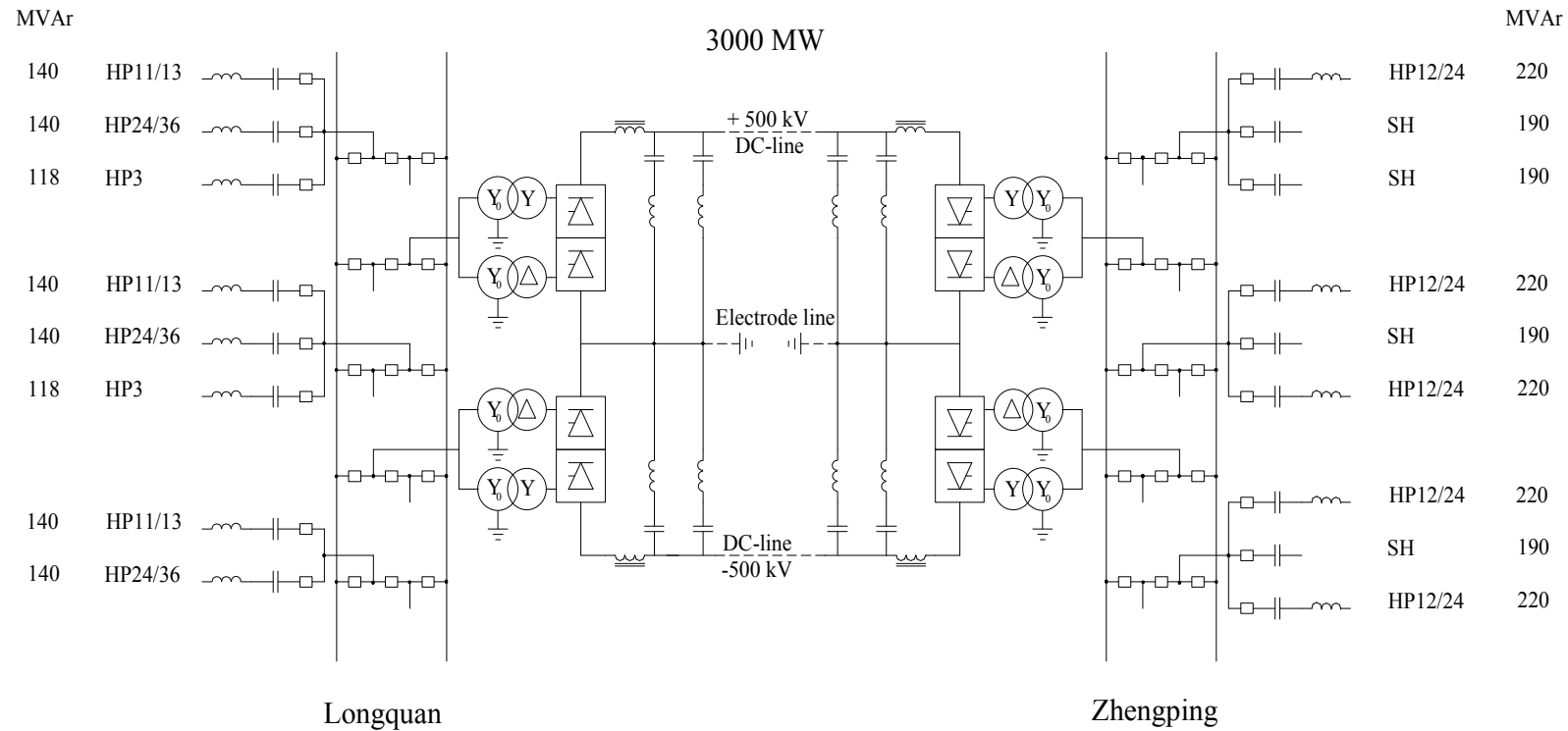Three Gorges - Changzhou HVDC Transmission Project



STUDY COMMITTEE B2, JWG B2-17/B4/C1

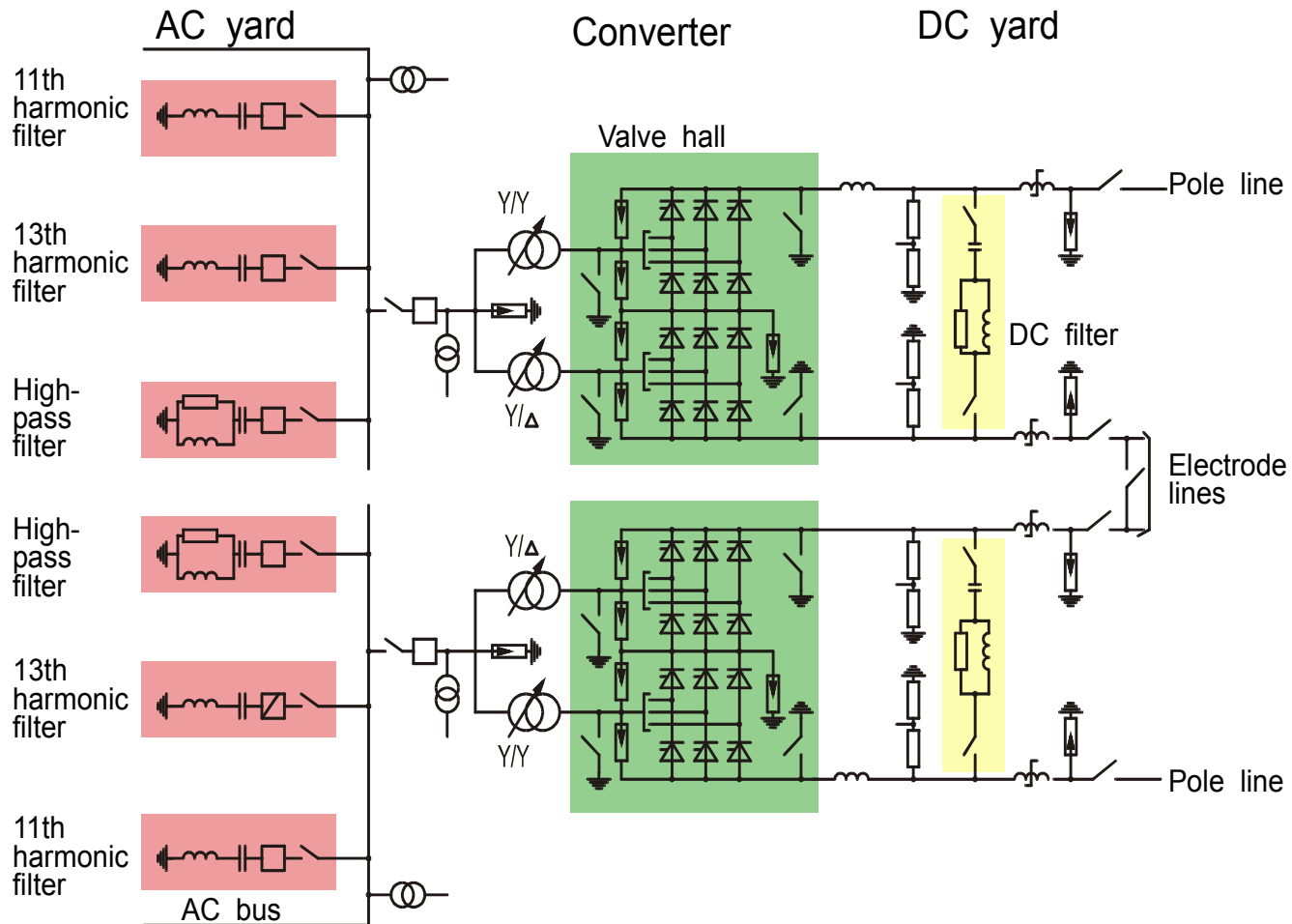
HVDC Transmission Configurations and Intermediate Stations



The Converter Station

STUDY COMMITTEE B2, JWG B2-17/B4/C1

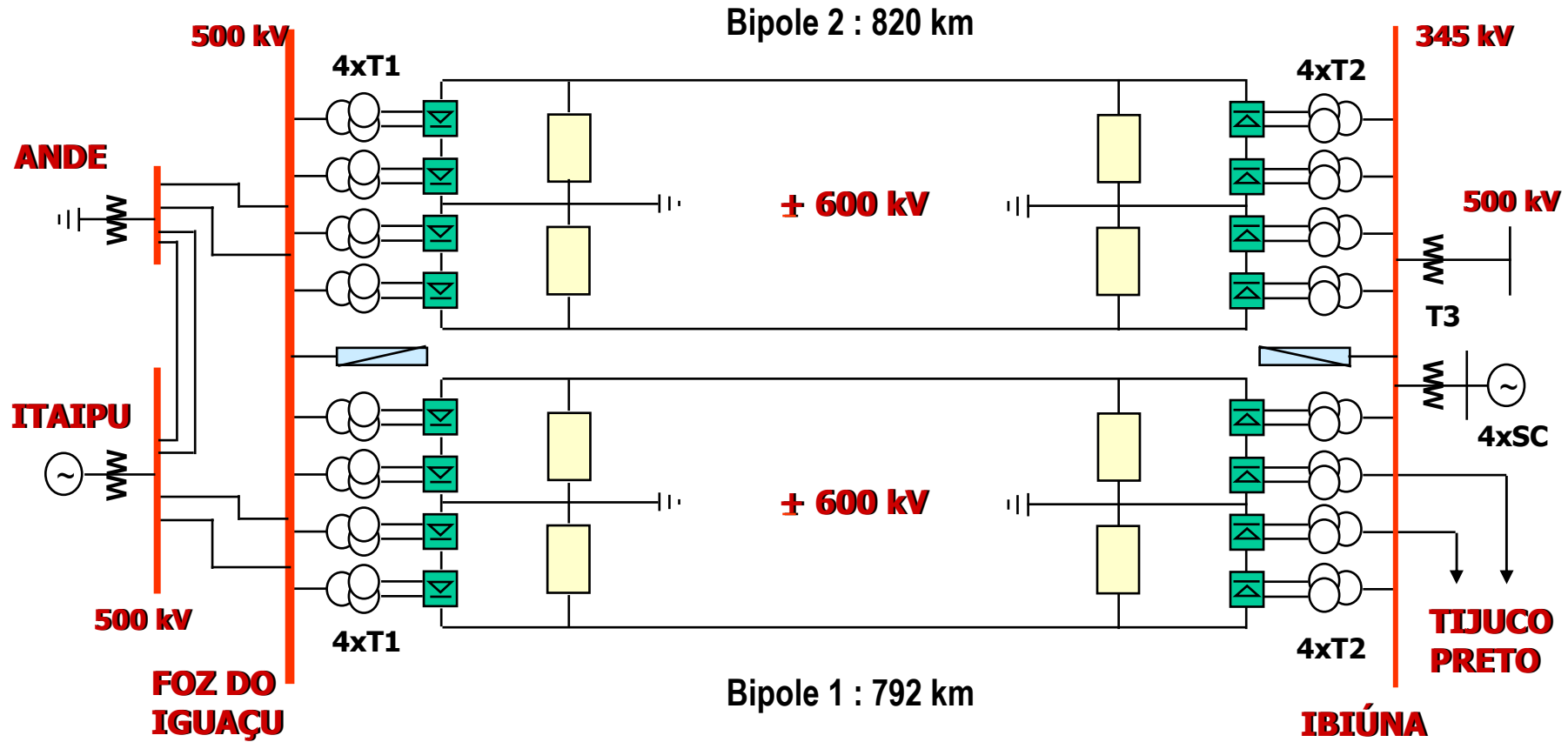
HVDC Transmission Configurations and Intermediate Stations



ITAIPU HVDC SYSTEM

Disjuntor de by-pass de conversor : By-pass Breaker

Câmaras SF₆
Externo compósito

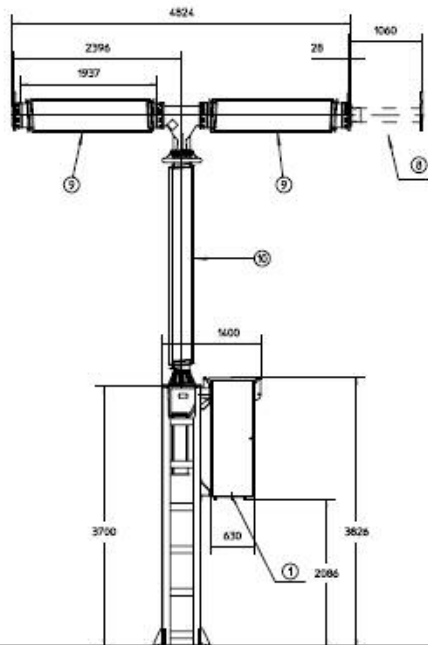

BPB de baixa

BPB de baixa


Metade da tensão
de pólo para
terra.

BPB de alta

Tensão de pólo
para terra.

Ambos:


Tensão de
conversora entre
contatos.

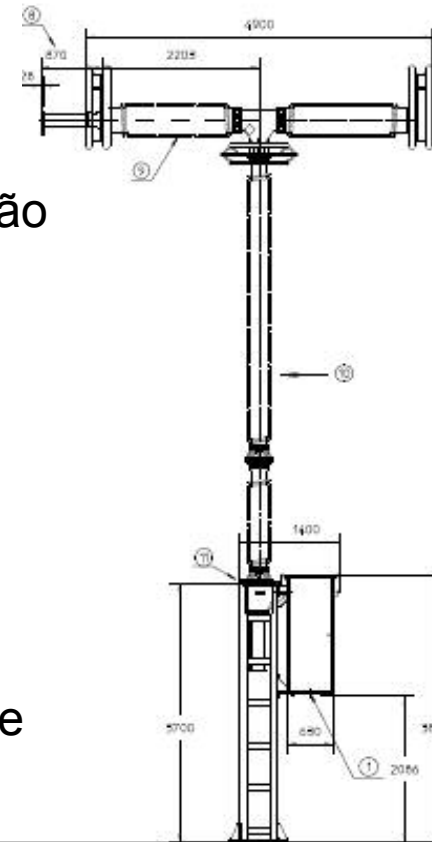

BPB de alta


STUDY COMMITTEE B2, JWG B2-17/B4/C1

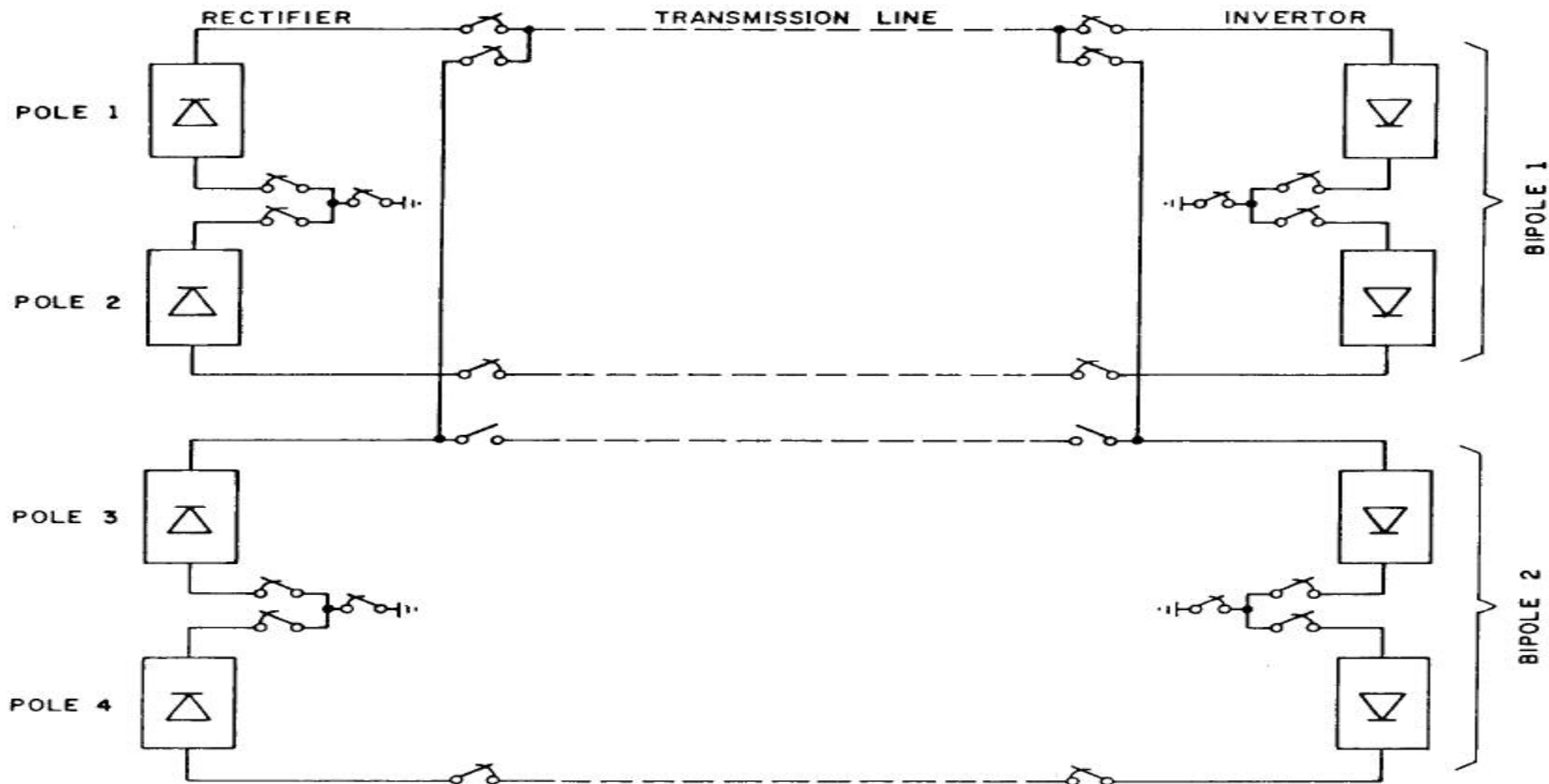HVDC Transmission Configurations and Intermediate Stations



ITAIPU HVDC SYSTEM : Pole Paralleling

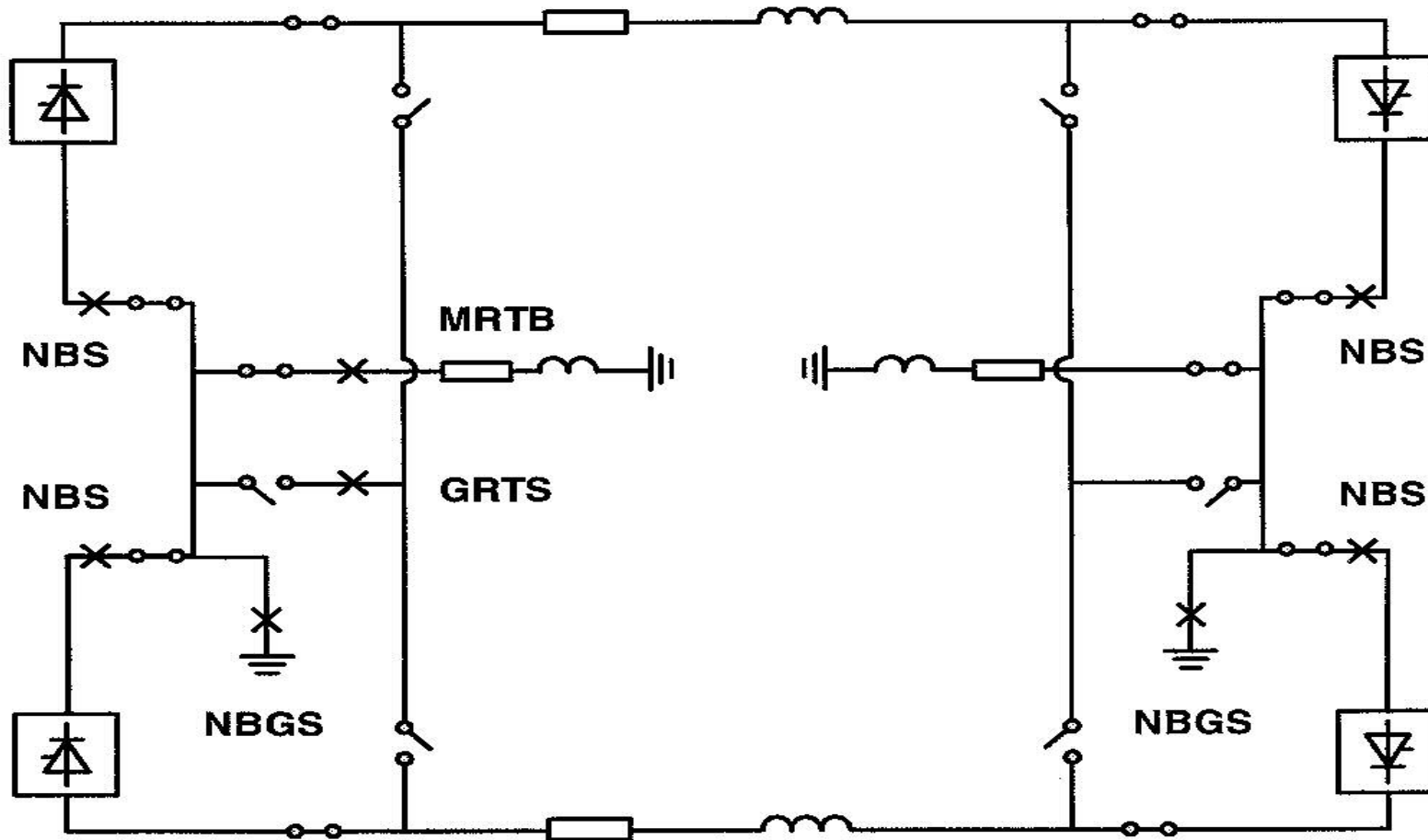
STUDY COMMITTEE B2, JWG B2-17/B4/C1
HVDC Transmission Configurations and Intermediate Stations



Transferência de retorno metálico : MRTB

Metallic Return Transfer Breaker

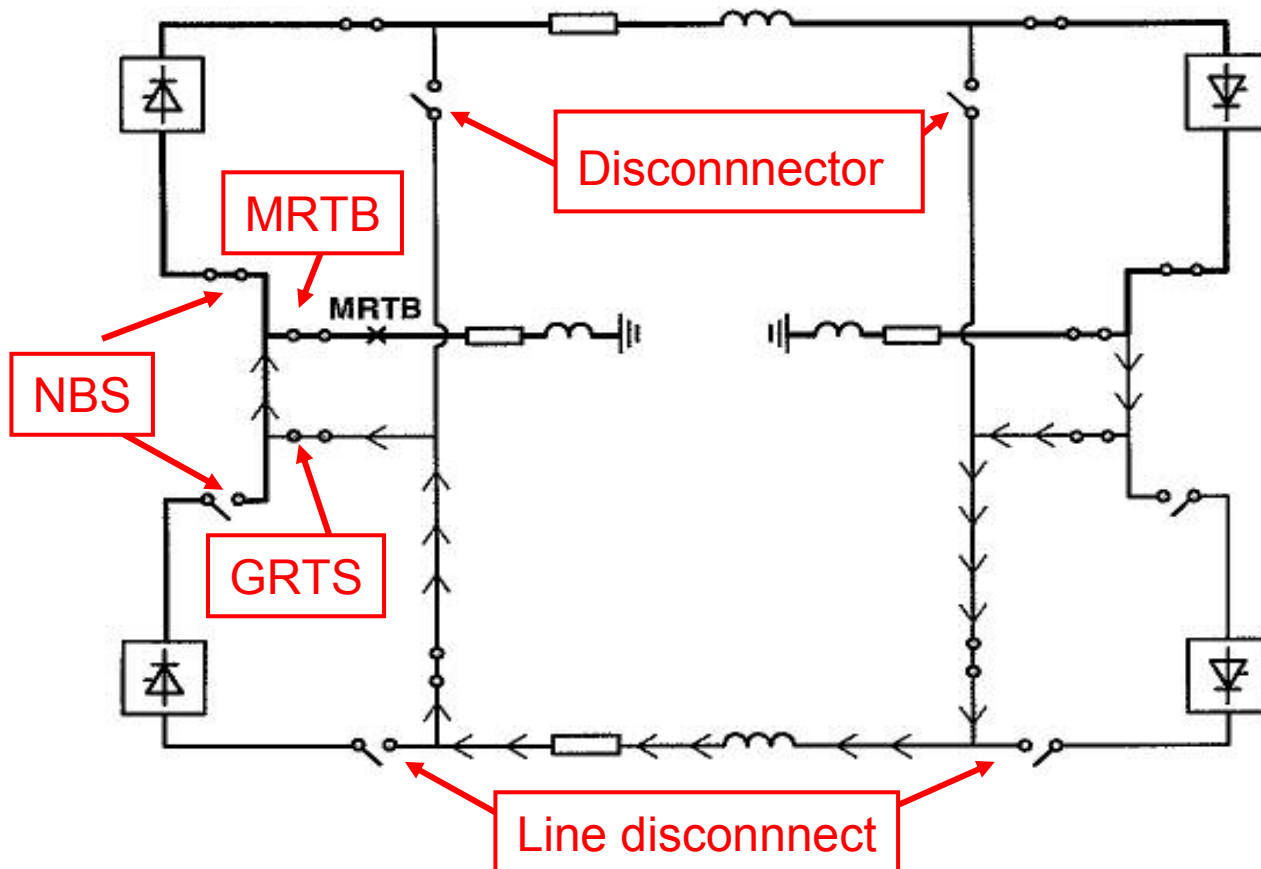Transferência de retorno metálico : MRTB usado para comutar o corrente do eletrodo de terra para o caminho de retorno metálico quando transmitindo em modo monopolar.



Metallic return is used to avoid ground currents during pole outages in the station, for example when carrying out maintenance.

STUDY COMMITTEE B2, JWG B2-17/B4/C1


HVDC Transmission Configurations and Intermediate



Componentes:

- Disjuntor SF₆
- Capacitor de Comutação
- Reator de Comutação
- Resistor Não-linear de ZnO

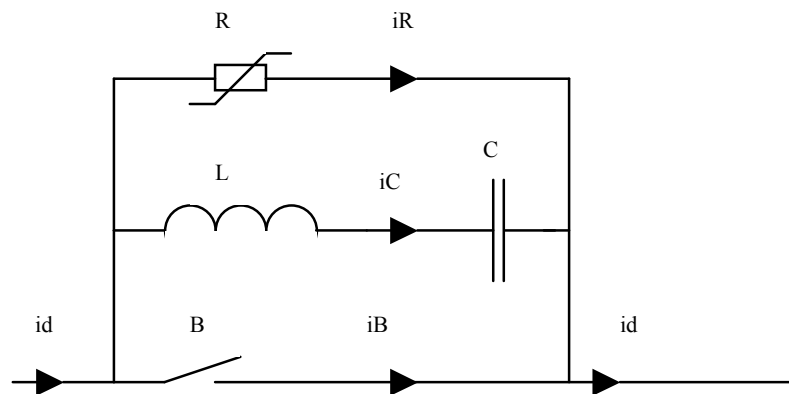Valores uma função do comprimento da linha e corrente. Hoje até 5 kA.



MRTB – Disjuntor de transferência metálico

STUDY COMMITTEE B2, JWG B2-17/B4/C1
HVDC Transmission Configurations and Intermediate Stations



Longquan 3000 MW, \pm 500 kV Valve Hall : Double-valves



STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations



Longquan 3000 MW


Large 500 kVac Station

3000 MW HVDC Rating

- Converter part relatively small
- One converter per pole
- Single phase two winding trafos
- Simple passive filter design
- Metallic Return
- Electrode Balancing



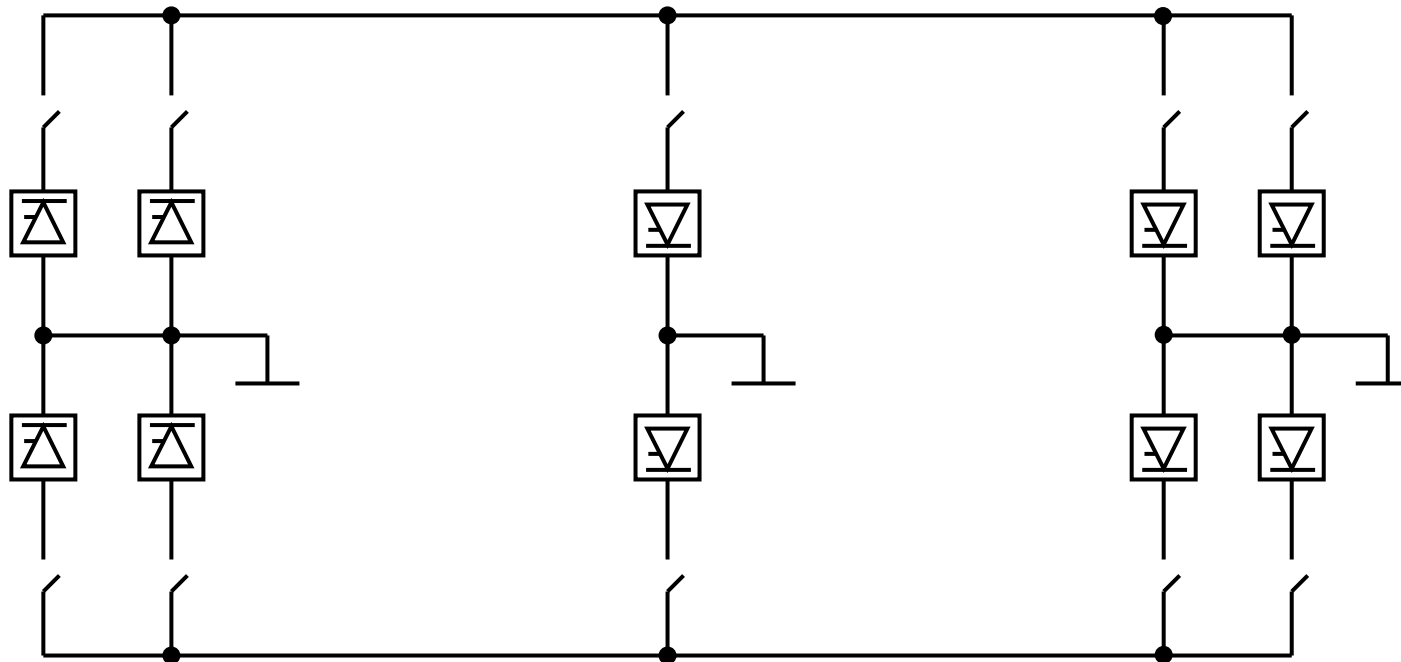Considerations regarding multi-terminal and “Tapping”.




Converters in parallel with classic CSC tapping:

Generation or Load

Requires active network for CSC

STUDY COMMITTEE B2, JWG B2-17/B4/C1

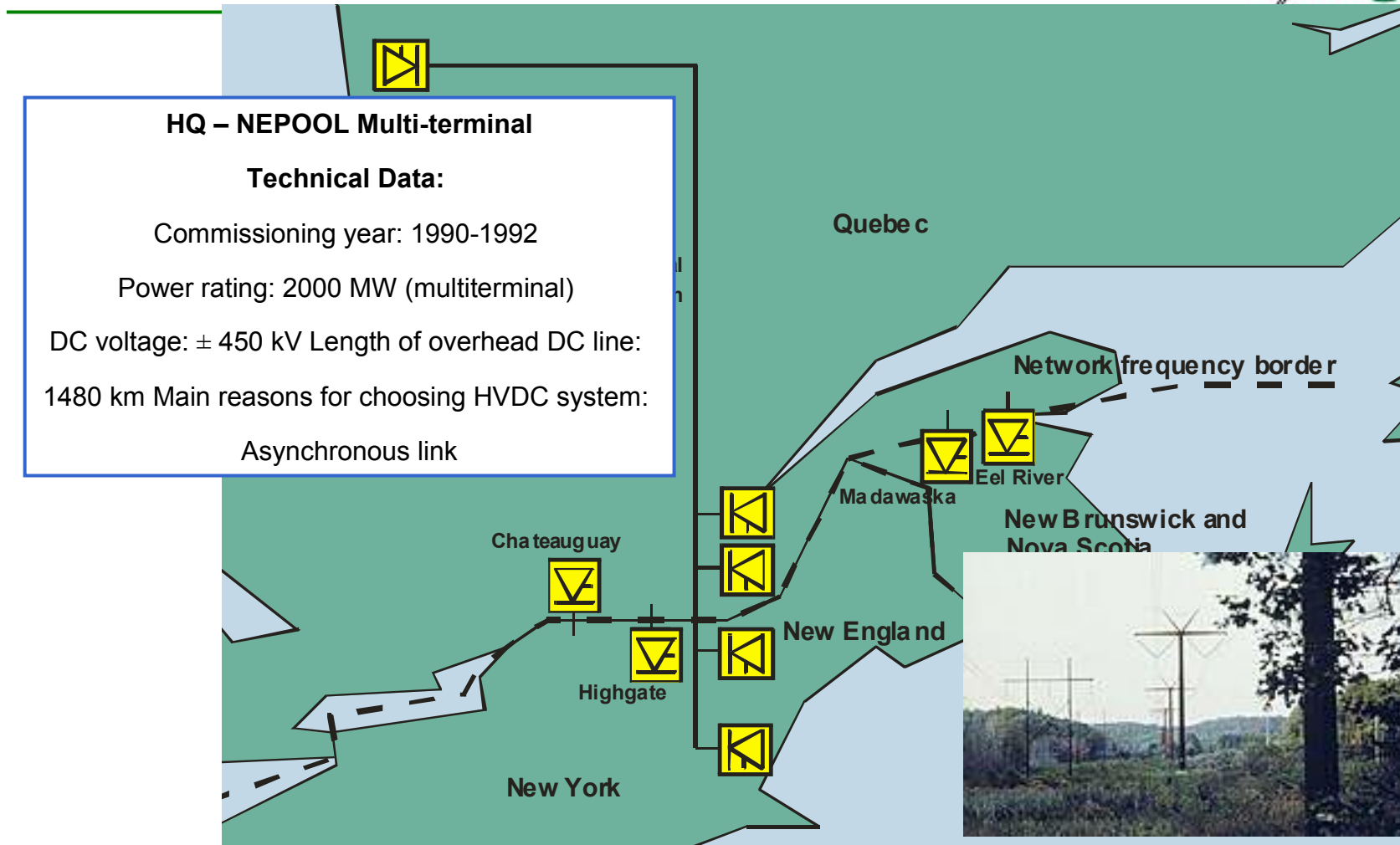
HVDC Transmission Configurations and Intermediate Stations



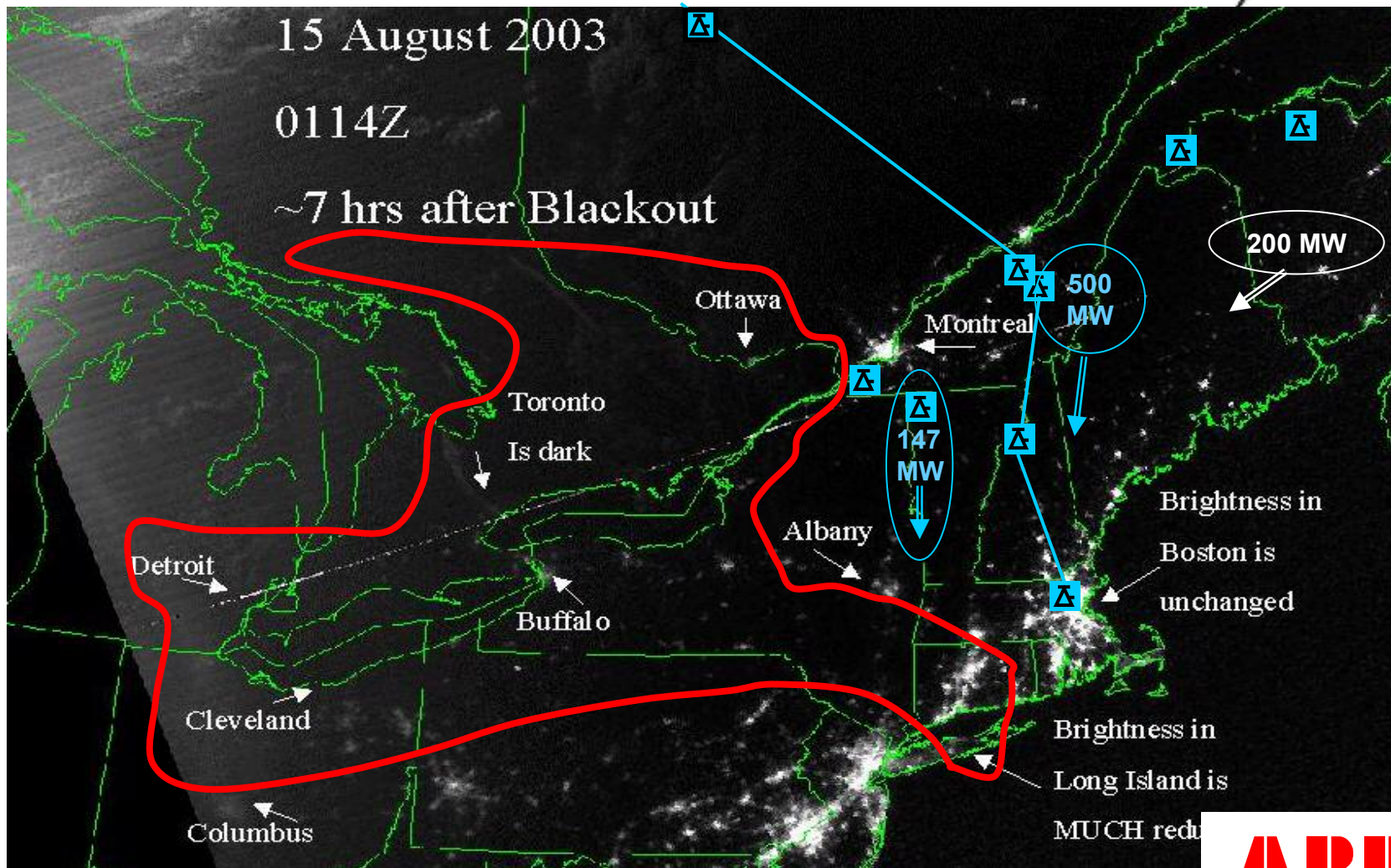Exemplo de Multi-terminal: Hydro Quebec – New England

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




Blackout Aug 14, 2003 Source: Public Power Weekly, August 25, 2003



STUDY COMMITTEE B2, JWG B2-17/B4/C1

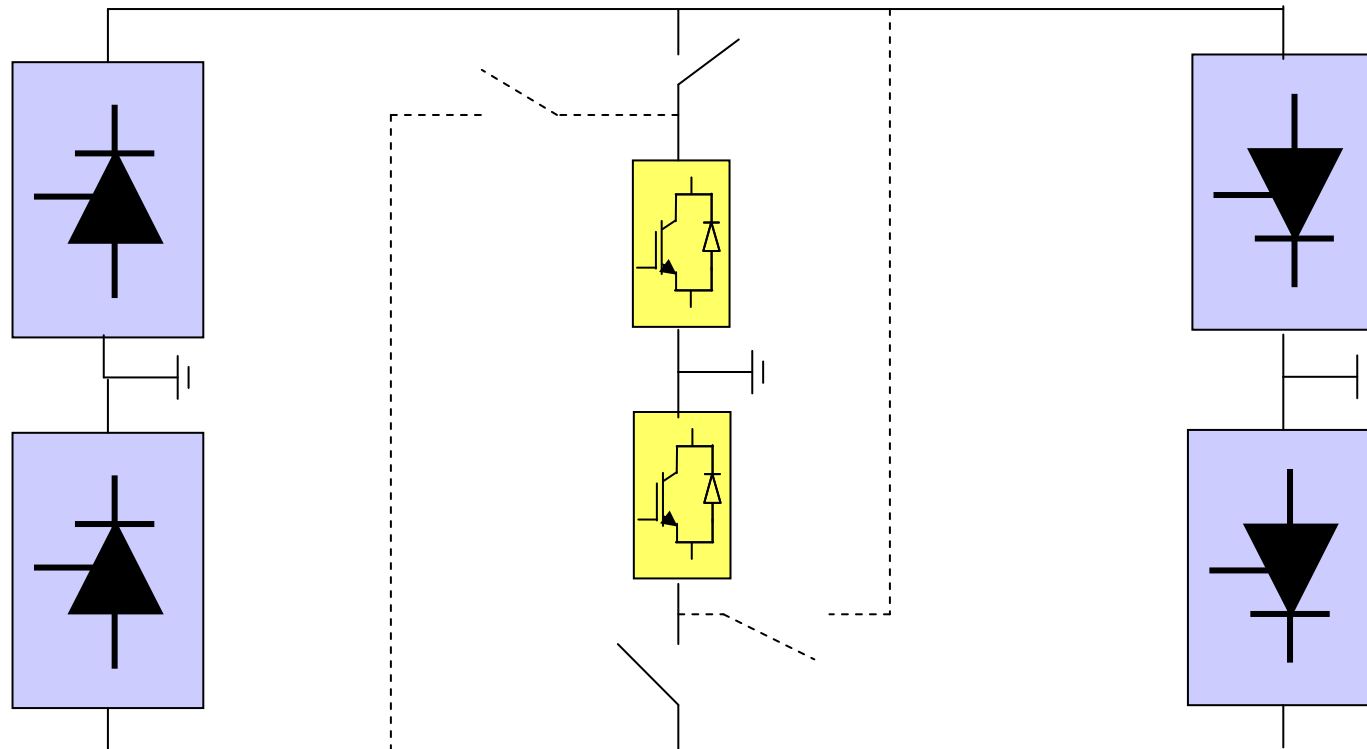
HVDC Transmission Configurations and Intermediate Stations



“Tapping” with bi-polar VSC converter:
Generation or Load
Can feed passive network or give “black start”.

STUDY COMMITTEE B2, JWG B2-17/B4/C1

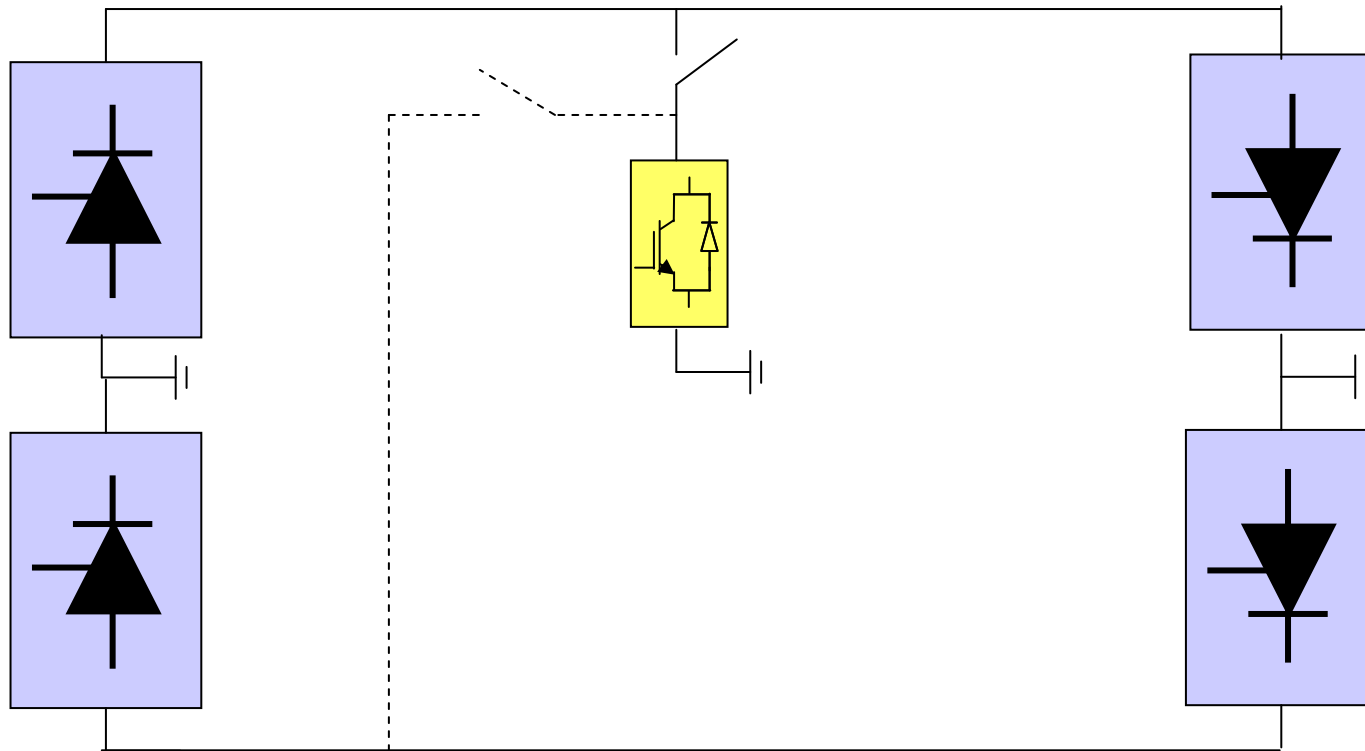
HVDC Transmission Configurations and Intermediate Stations



“Tapping” with mono-polar VSC converter
For smaller loads (100 MW, 500 kV)
Note: Ground current

STUDY COMMITTEE B2, JWG B2-17/B4/C1

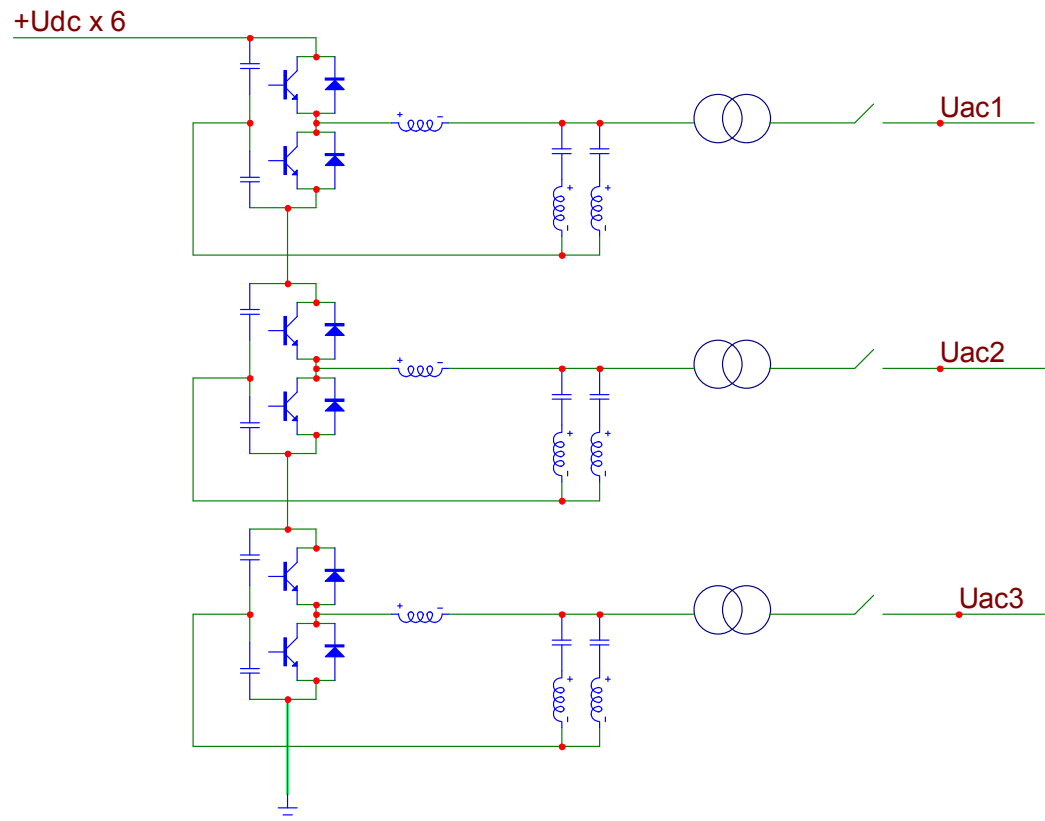HVDC Transmission Configurations and Intermediate Stations



“Tapping” with VSC converter.
One pole connected to line voltage

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




Voltage C.C.	500 A	1000 A	1500 A
+/- 480 kV	M1- 2x95 MVA	M2- 2x190 MVA	M3- 2x285 MVA
+/-900 kV	M4- 2x178 MVA	M5- 2x356 MVA	M6- 2x535 MVA


“Tapping” with VSC converter.
Available ratings

STUDY COMMITTEE B2, JWG B2-17/B4/C1

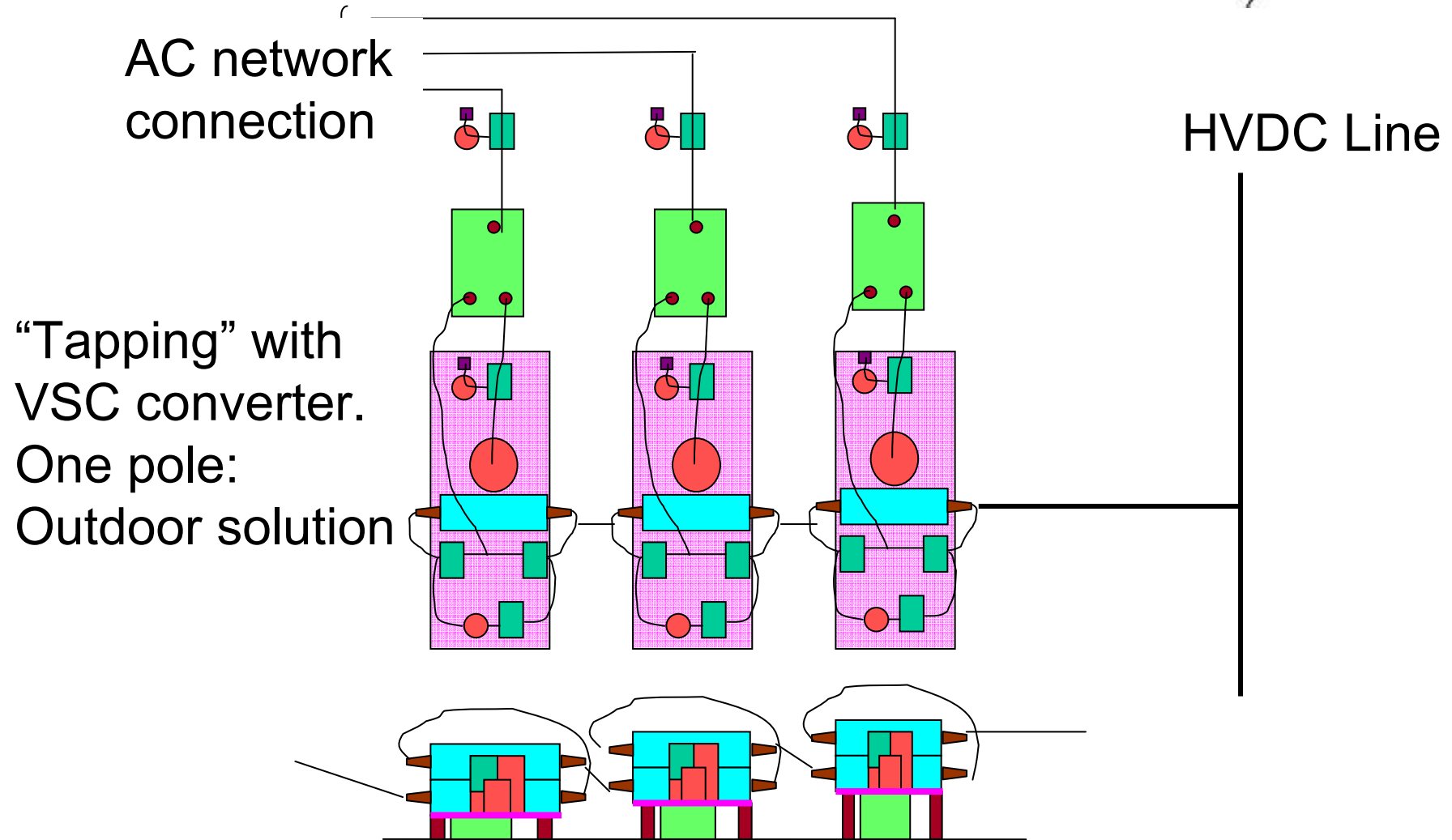HVDC Transmission Configurations and Intermediate Stations





Voltage source converters (VSCs)

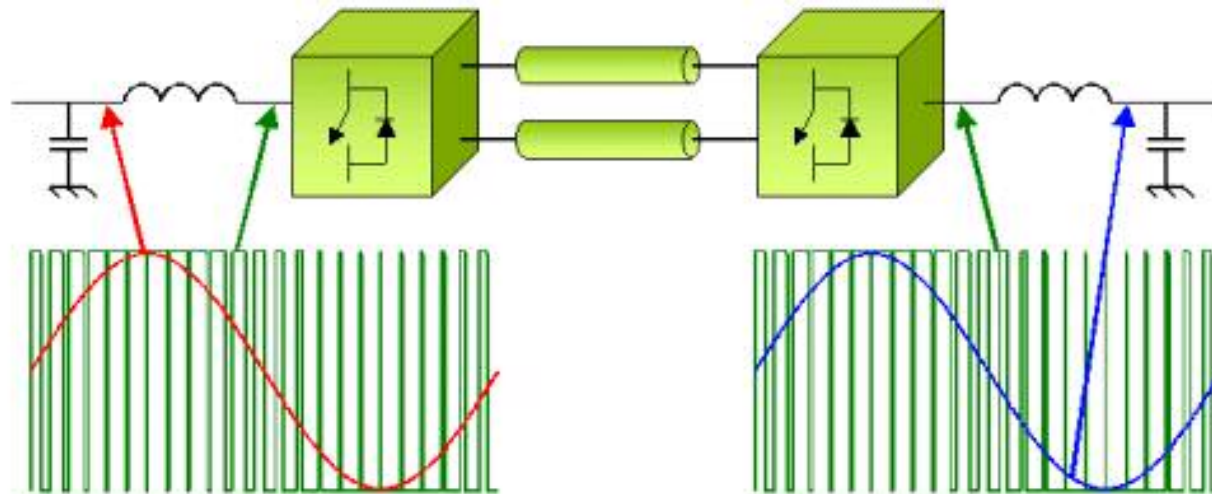

- IGBT based Voltage Source Converter
 - Successful technology in industrial drives
- Fast, independent control of active and reactive power flows
- High switching frequency, compact filters, no synchronous condenser
- HVDC Light Cable™: Flexible, cost-effective extruded polymer HVDC cable

VSC station components

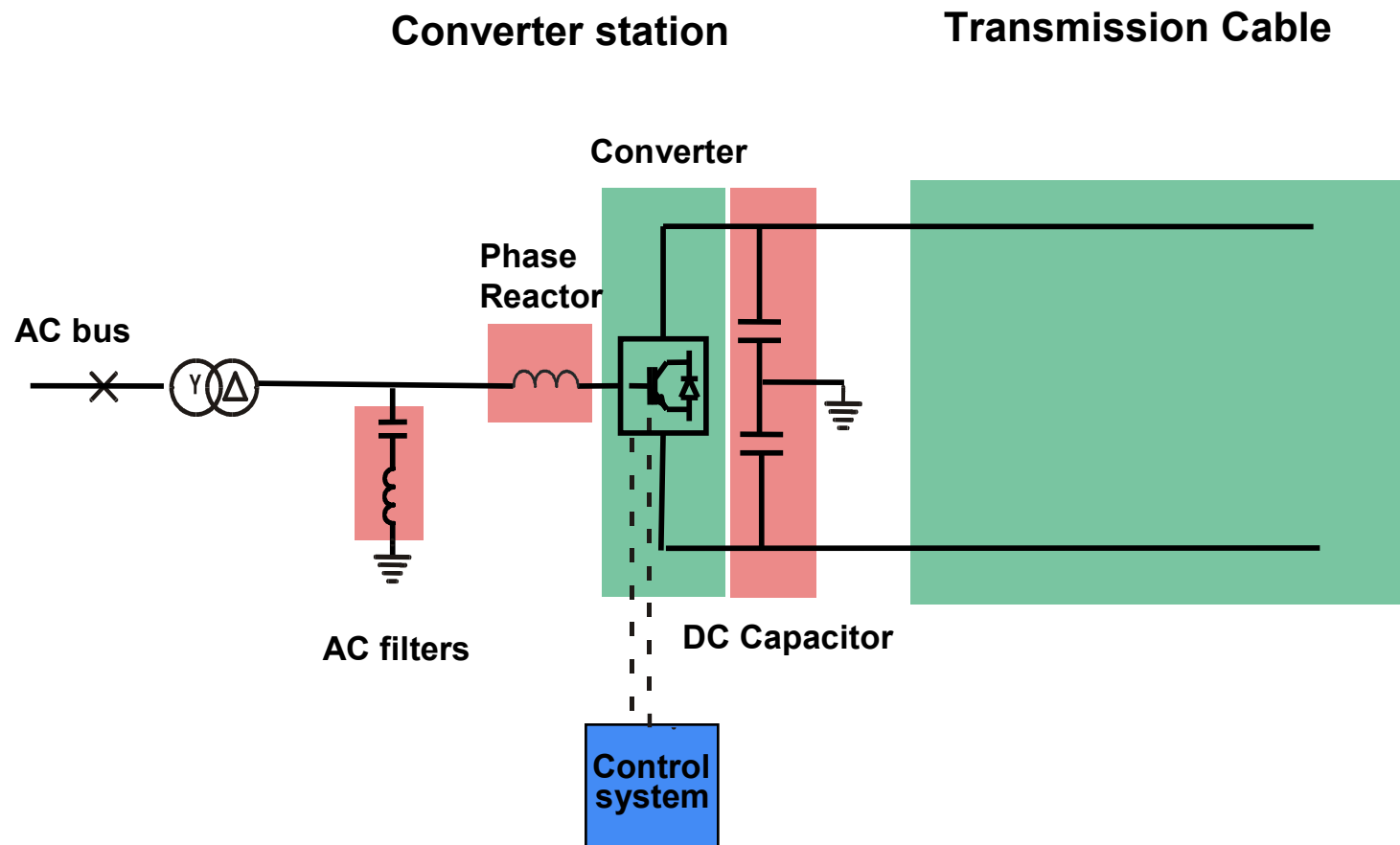


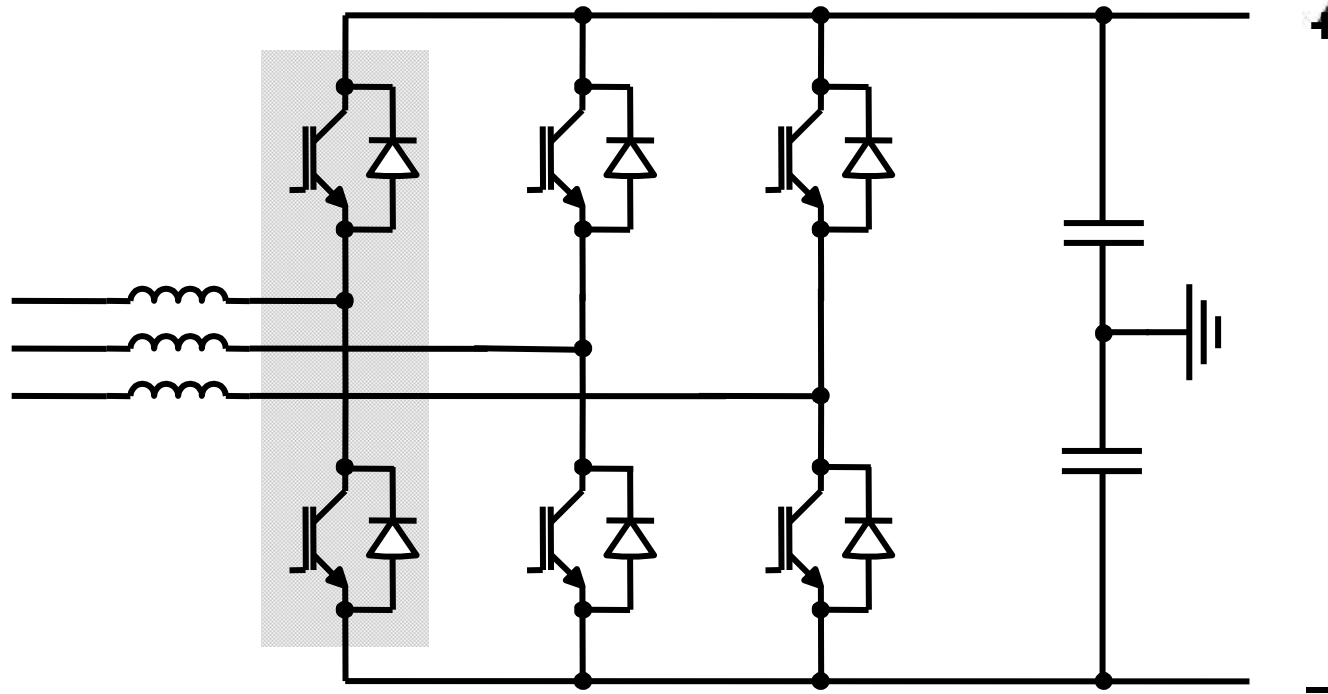

Valves {
Commutation between valves in same phase
Reverse voltage capability only
Conducts current in both directions

VSC converter with IGBTs and PWM

VSCs in bipolar configuration

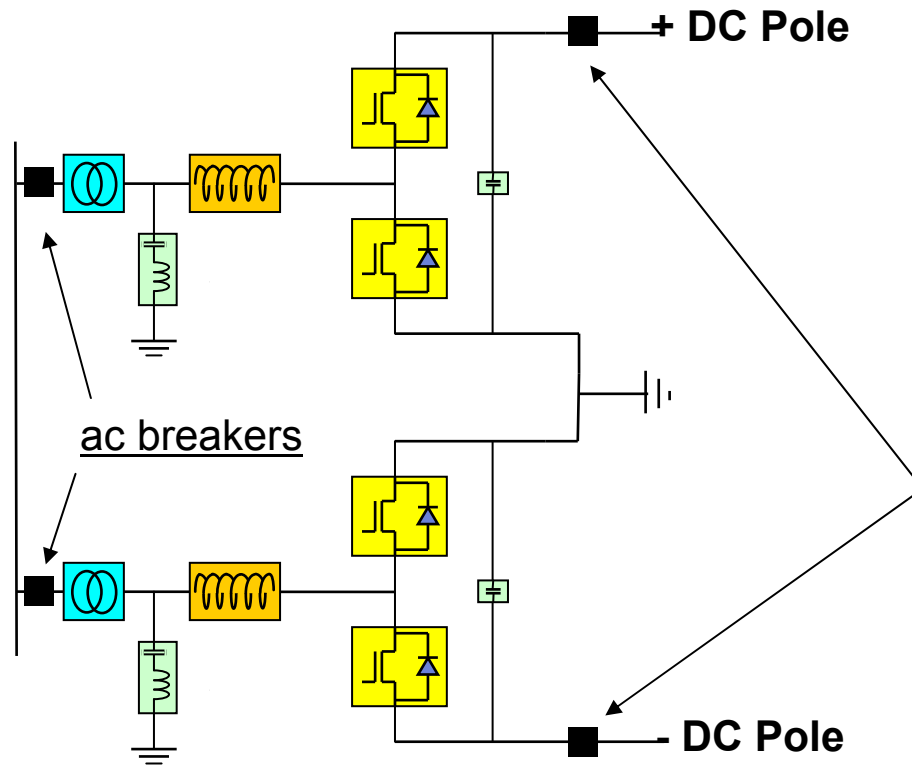

When using OH Line


DC breakers must be installed in both ends.

At DC line fault the following sequence must be initiated:



- Open ac breakers in both ends of faulty pole (to stop injection of fault current).
- After around 200 ms open the dc breakers in both ends.
- After around 400 ms close the ac breakers and run both converters in SVC mode
- after around 500 ms close the dc breakers and start power transmission.
- **Total about one second**

STUDY COMMITTEE B2, JWG B2-17/B4/C1

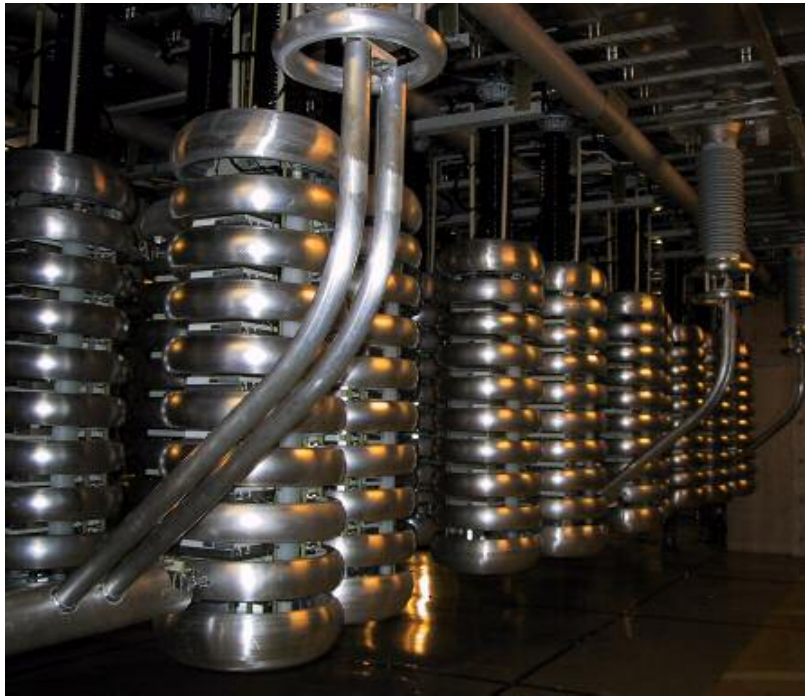HVDC Transmission Configurations and Intermediate Stations



Converter valves in module

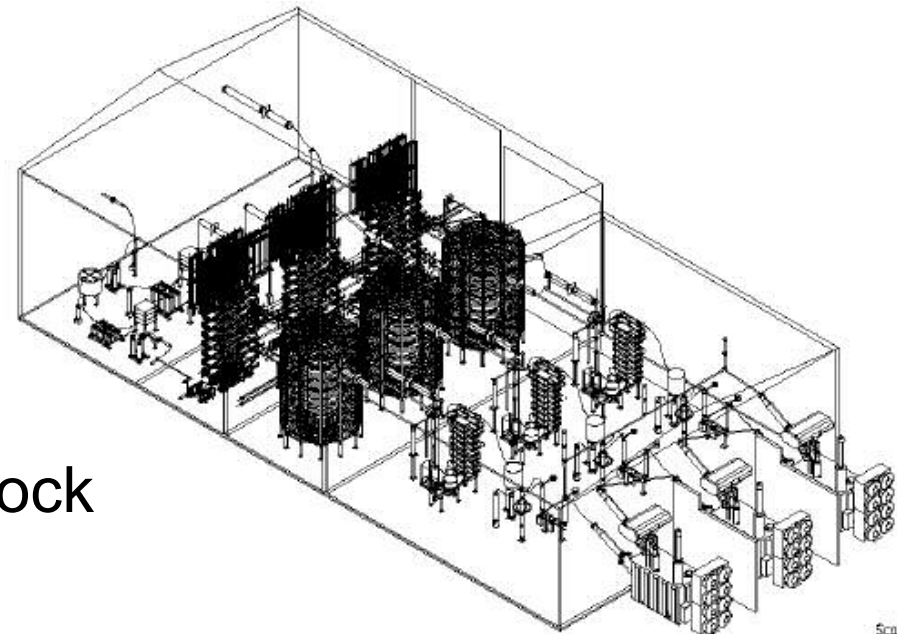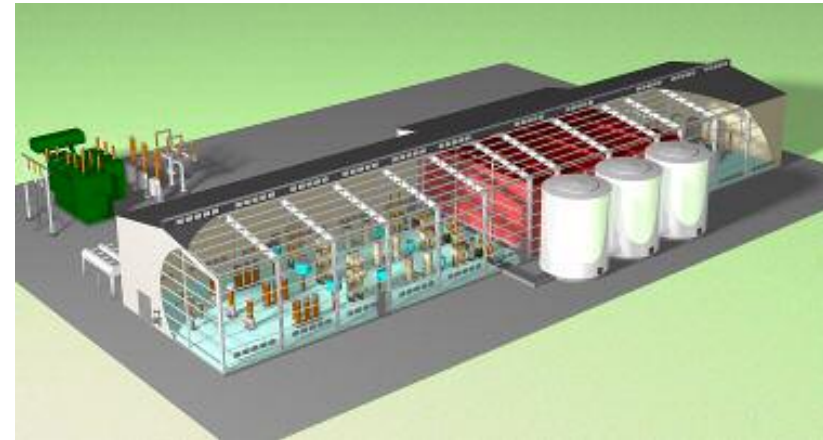

VSC 300MW block



STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations




JWG B2.17 has at 12 converter ratings/configurations to consider:


	1	2	3	4	5	6	7	8	9	10	11	12
Bipolar	750 MW	750 MW	750 MW	750 MW	1500 MW	1500 MW	3000 MW	3000 MW	3000 MW	6000 MW	6000 MW	6000 MW
Rating	± 300 kV	± 300 kV	± 300 kV	± 500 kV	± 300 kV	± 500 kV	± 500 kV	± 600 kV	± 800 kV	± 600 kV	± 800 kV	± 800 kV
conv/pole	VSC	1x6pulse	1	1	1	1	1	1	1	2 par	2 ser	2 par

Bipole	750 MW	1500 MW	3000 MW	6000 MW
750 km	± 300 kV	± 300 kV ± 500 kV	± 500 kV	
1500 km	± 300 kV ± 500 kV	± 500 kV	± 500 kV ± 600 kV ± 800 kV	± 600 kV ± 800 kV
3000 km			± 500 kV ± 600 kV ± 800 kV	± 600 kV ± 800 kV


- Many configurations for lower powers
- One converter per pole intermediate
- Series vs parallel for high powers

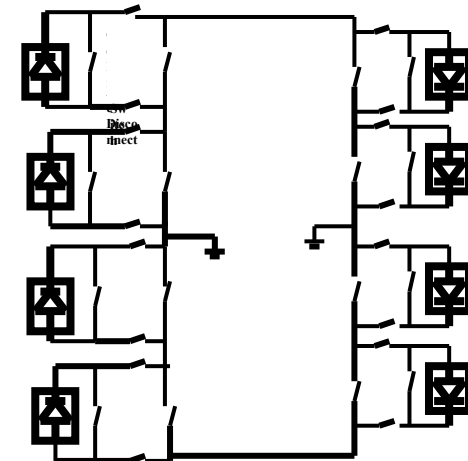

Case 11

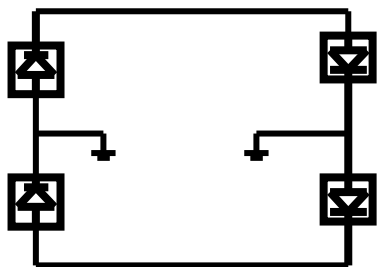

Cases 3 to 9

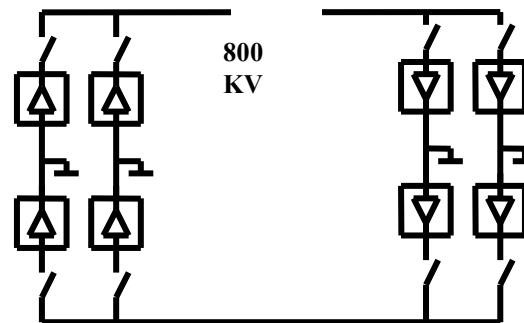

Cases 10 and 12

STUDY COMMITTEE B2, JWG B2-17/B4/C1

HVDC Transmission Configurations and Intermediate Stations



Tutorial of JWG-B2/B4/C1.17 on HVDC Transmission Systems –
Design and Economics
Converter Configurations – John Graham, ABB Brasil

john.graham@br.abb.com